



Under Construction: VA7FI is editing this section, please do not edit it until this notice is taken down.

Electronics

RLC Addition

	Series	Parallel
Resistor, R [Ω]	$R = R_1 + R_2$	
Inductor, L [H]		
Capacitor, C [F]		

Questions

