



Under Construction: VA7FI is editing this section, please do not edit it until this notice is taken down.

Electronics

RLC Addition

	Series	Parallel
Resistor, R [Ω]	$\$R = R_1 + R_2\$$	
Inductor, L [H]	$\$L = L_1 + L_2\$$	
Capacitor, C [F]	$\$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}\$$	

Questions

