



**Under Construction:** VA7FI is editing this section, please do not edit it until this notice is taken down.

# Electronics

## RLC Impedance



Impedance [ $\Omega$ ]	Low Frequency	Medium Frequency	High Frequency
Resistance, R	Doesn't depend on frequency		
Inductive Reactance $X_L = 2\pi f L$	Low	Medium	High
Capacitive Reactance $X_C = \frac{1}{2\pi f C}$	High	Medium	Low

## RLC Addition

	Series	Parallel
Resistor, R [ $\Omega$ ]	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
	$R = R_1 + R_2$	$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$
Inductor, L [H]	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
	$L = L_1 + L_2$	$\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2}$
Capacitor, C [F]	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
	$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$	$C = C_1 + C_2$

## Questions

