



**Under Construction:** VA7FI is editing this section, please do not edit it until this notice is taken down.

# Electronics

In this section we'll discuss the three basic electronic components:

Name	Property	Unit	Symbol
Resistor (R)	Resistance	Ohm ( $\Omega$ )	
Inductor (L)	Inductance	Henry (H)	
Capacitor (C)	Capacitance	Farad (F)	


## Resistor

The easiest component to start with is the resistor.

“

In electronic circuits, resistors are used to reduce current flow, adjust signal levels, to divide voltages, bias active elements, and terminate transmission lines, among other uses. High-power resistors that can dissipate many watts of electrical power as heat, may be used as part of motor controls, in power distribution systems, or as test loads for generators. Fixed resistors have resistances that only change slightly with temperature, time or operating voltage. Variable resistors can be used to adjust circuit elements (such as a volume control or a lamp dimmer), or as sensing devices for heat, light, humidity, force, or chemical activity.” [Wikipedia: Resistor](#)

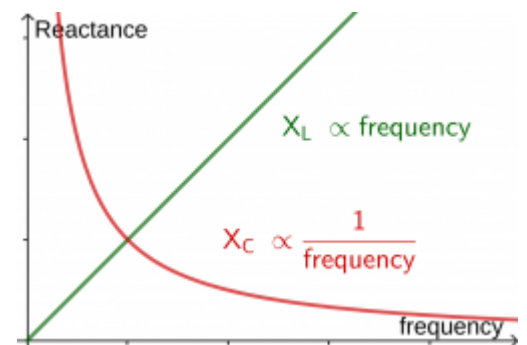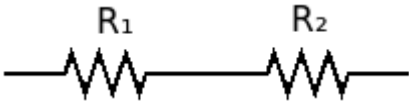
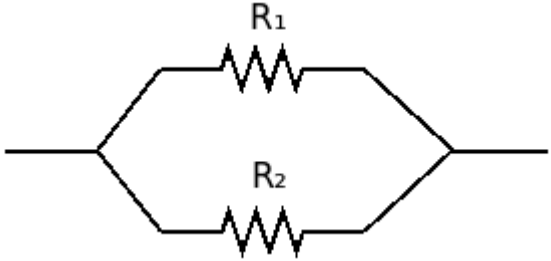

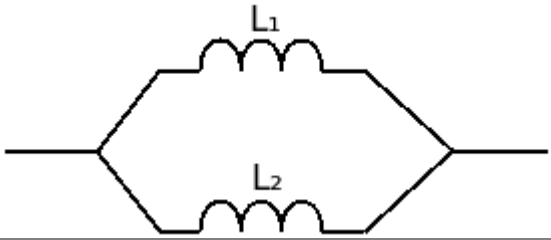
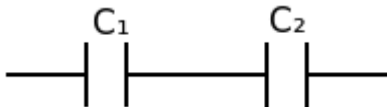
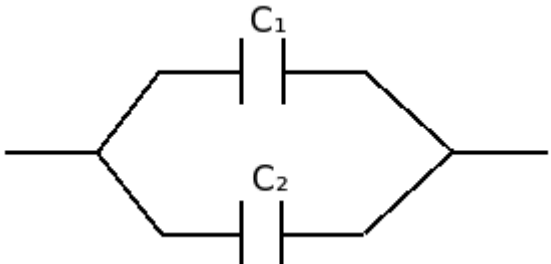
## RLC Impedance



Impedance ( $\Omega$ )	Low Frequency	Medium Frequency	High Frequency
Resistance, R	Doesn't depend on frequency		
Inductive Reactance $X_L = 2\pi f L$	Low	Medium	High

Impedance ( $\Omega$ )	Low Frequency	Medium Frequency	High Frequency
Capacitive Reactance $X_C = \frac{1}{2\pi f C}$	High	Medium	Low

## RLC Addition

	Series	Parallel
Resistor, R [ $\Omega$ ]		
	$R = R_1 + R_2$	$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$
Inductor, L [H]		
	$L = L_1 + L_2$	$\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2}$
Capacitor, C [F]		
	$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$	$C = C_1 + C_2$

## Questions

