



Under Construction: VA7FI is editing this section, please do not edit it until this notice is taken down.

Electronics

In this section we'll discuss the three basic electronic components:

| Name | Property | Unit | Symbol | Picture | Source |
|---------------|-------------|------------------|--------|---------|---------------------------|
| Resistor (R) | Resistance | Ohm (Ω) | | | Resistor |
| Inductor (L) | Inductance | Henry (H) | | | Inductor |
| Capacitor (C) | Capacitance | Farad (F) | | | Capacitor |

Resistor

The easiest component to start with is the resistor.

“

In electronic circuits, resistors are used to reduce current flow, adjust signal levels, divide voltages, bias active elements, and terminate transmission lines, among other uses. High-power resistors that can dissipate many watts of electrical power as heat [...] or as test loads for generators. Fixed resistors have resistances that only change slightly with temperature, time or operating voltage. Variable resistors can be used to adjust circuit elements (such as a volume control or a lamp dimmer), or as sensing devices for heat, light, humidity, force, or chemical activity.” [Wikipedia: Resistor](#)





RLC Impedance



| Impedance (Ω) | Low Frequency | Medium Frequency | High Frequency |
|--|-----------------------------|------------------|----------------|
| Resistance, R | Doesn't depend on frequency | | |
| Inductive Reactance $X_L = 2\pi f L$ | Low | Medium | High |
| Capacitive Reactance $X_C = \frac{1}{2\pi f C}$ | High | Medium | Low |

RLC Addition

| | Series | Parallel |
|--------------------------|-----------------|---|
| | | |
| Resistor, R [Ω] | $R = R_1 + R_2$ | $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$ |

| | Series | Parallel |
|------------------|---|---|
| |  |  |
| Inductor, L [H] | $L = L_1 + L_2$ | $\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2}$ |
| |  |  |
| Capacitor, C [F] | $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$ | $C = C_1 + C_2$ |

Questions

